Broadmayne First School Knowledge Organiser

Science Focus Electricity Year 4 Autumn Term 2

Key Knowledge				
What is electricity?	 Electricity is a source of power that is generated by coal, gas, oil, wind or solar power. Electrical energy can be turned into heat, light, movement and sound. Electricity is very dangerous and must be treated very carefully 			
What are common electrical appliances?	 An appliance is something that needs to be plugged into an electrical circuit to work. It will not work if it is not plugged in. Common appliances include television, washing machine, hairdryer, iron, gaming console, lights, microwave. Some appliances also run on batteries. These appliances can be charged up and then used without a plug, for example, mobile phone, tablet, toothbrush. 			
Electrical circuits Buzzer Buzzer Bulb Switch	 Electricity flows through the components of a complete electrical circuit. A circuit must have a power source (usually a battery), wires to connect the components and different components such as light bulbs, buzzers or motors. There cannot be any gaps in the circuit, otherwise the electricity cannot flow through. 			
Switches	 A switch can be used to create a gap in a circuit so that the components can be turned ON and OFF. When the switch is open, there is a gap in the circuit and the electricity cannot flow around the circuit. When the switch is closed, there are no gaps in the circuit and the electricity flows around the circuit. 			
Electrical conductors	 Electrical conductors let electricity pass through them easily. Many metals are good conductors of electricity. 			
Electrical insulators	 Electrical insulators do not allow electricity to pass through them. Wood, plastic, glass and rubber are examples of good insulators. Electrical insulators can be used to cover materials that carry electricity. 			

Spelling (Key Vocab)	Definition		
appliance	something that needs to be plugged in to work.		
circuit	a complete route that electricity can flow around.		
component	part of a circuit such as battery, bulb, wires		
conductor	allows electricity to pass through		
insulator	does not allow electricity to pass through		
switch	Can create a gap by turning the circuit on and off		

Planned experiences

Set up circuits and predict whether the bulb will light or not.

Set up circuits and explore how to make a bulb shine brighter.

Set up a circuit and test whether materials are conductors or insulators.

Visitor to discuss electrical safety.